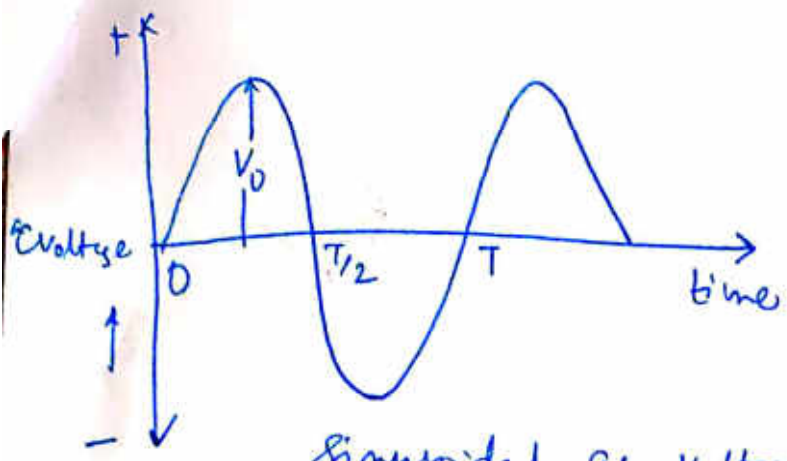


Alternating Currents



sinusoidal ac voltage

passes through a complete cycle of changes both in magnitude and direction at regular intervals of time.

$$v = V_0 \sin \omega t$$

$$v = V_0 \cos \omega t \quad V_0 \rightarrow \text{peak value}$$

$$i = I_0 \sin(\omega t + \phi)$$

Steady dc circuit current & voltage remain in phase

Avg or mean value of ac

$$I_{\text{ave}} = \frac{1}{T/2} \int_{t_1}^{t_1 + T/2} i(t) dt \quad \text{half cycle}$$

Simple sinusoidal current $i = I_0 \sin \omega t$

$$I_{\text{ave}} = \frac{1}{T/2} \int_0^{T/2} I_0 \sin \omega t \cdot dt = \frac{2I_0}{T\omega} [-\cos \omega t]_0^{T/2} = \frac{2I_0}{\pi} \left[\because \omega T = \frac{2\pi}{T} \right]$$

$$V_{\text{ave}} = \frac{2V_0}{\pi}$$

$$I_{\text{ave}} \cdot \frac{T}{2} = \int_{t_1}^{t_1 + T/2} i(t) dt$$

Root mean square or eff. value of ac

$$I_r = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

Heat produced by ac in a resistance R over a time period T

$$\int_0^T i^2(t) \cdot R \cdot dt = I_r^2 \cdot R \cdot T$$

for $i = I_0 \sin \omega t$

$$I_r^2 = \frac{1}{T} \int_0^T I_0^2 \sin^2 \omega t \, dt = \frac{I_0^2}{2T} \int_0^T (1 - \cos 2\omega t) \, dt$$

$$= \frac{I_0^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^T = \frac{I_0^2}{2}$$

Therefore, $I_r = \frac{I_0}{\sqrt{2}}$, $V_r = \frac{V_0}{\sqrt{2}}$

When we speak of 220V ac supply we mean its rms value. Thus, peak value of a 220V ac supply is

$$V_0 = \sqrt{2} \times V_r = \sqrt{2} \times 220V = 311V.$$

Form factor

The ratio of an rms value to the avg value of a is called its form factor (K_f). For a pure sinusoidal ac,

$$K_f = \frac{I_r}{I_{av}} = \frac{I_0/\sqrt{2}}{2I_0/T} = 1.11$$

Form factor gives an idea about the wave shape. Any deviation in the value of K_f from 1.11 indicates deviation from sinusoidal nature.

Peak factor

The ratio of the peak value to the rms value of any ac waveform is called its peak factor. For a pure sinusoidal ac,

$$\text{peak factor } (K_p) = \frac{I_0}{I_0/\sqrt{2}} = \sqrt{2}.$$

Power in ac circuits

$$p(t) = v(t) \cdot i(t)$$

$p(t)$ may be +ve, 0 or -ve.

+ve: circuit is receiving en from the source

-ve: source " " " " " " circuit.

$$\text{avg power } P = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt$$

$$v(t) = V_0 \sin \omega t \quad \& \quad i(t) = I_0 \sin(\omega t + \phi)$$

$$\therefore P = \frac{V_0 I_0}{T} \int_0^T \sin \omega t \cdot \sin(\omega t + \phi) dt = \frac{V_0 I_0}{2T} \int_0^T [\cos \phi - \cos(2\omega t + \phi)] dt$$

$$= \frac{V_0 I_0}{2} \cos \phi = \frac{V_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \cos \phi = V_r \cdot I_r \cdot \cos \phi$$



power factor

Real power = apparent power \times power factor

If in any case voltage and current differ in phase by 90° then $\cos \phi = 0$ and hence no power is dissipated in the circuit. The current flowing in such circuits is called wattless current.

Current flowing through a pure inductor or a pure capacitor is a wattless current.

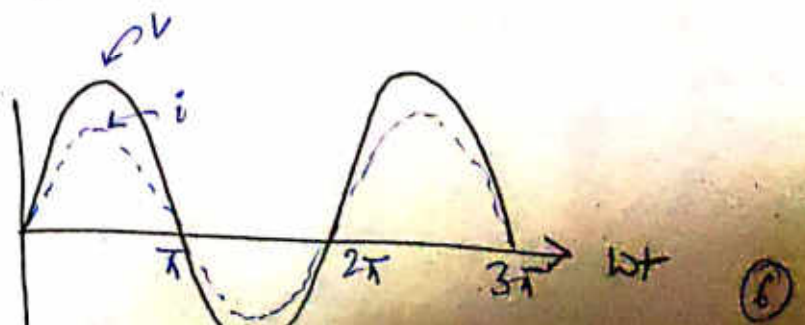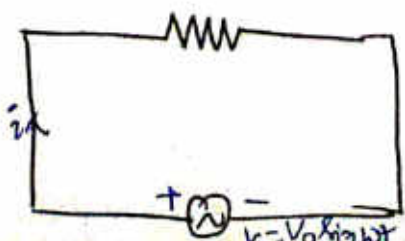Current-Voltage Relationship in Pure Resistance, Inductor and Capacitor



$$v = Ri \text{ or } i = \frac{V_0}{R} \sin \omega t = I_0 \sin \omega t$$

in pure resistance current is in phase with the app. voltage.

$$P = V_r \cdot I_r \cos \phi = \frac{V_0 I_0}{2} \cos 0 = I_r^2 R$$


(ii) Pure inductance

$\omega L \sim R$


$$v = V_0 \sin \omega t = L \frac{di}{dt} \text{ or } di = \frac{V_0}{L} \sin \omega t dt$$

$$i = \frac{V_0}{L} \int \sin \omega t dt = -\frac{V_0}{\omega L} \cos \omega t = -\frac{V_0}{\omega L} \sin(\omega t - \pi/2) = \frac{V_0}{\omega L} \sin(\omega t - \pi/2)$$

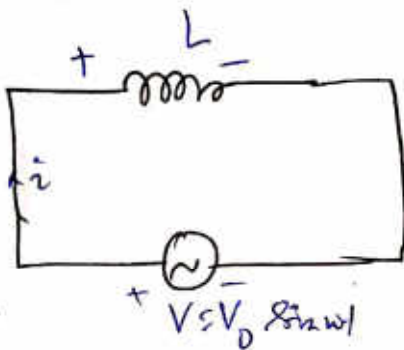$I_0 = \frac{V_0}{\omega L}$, $\omega L \rightarrow$ inductive reactance




Choke coil

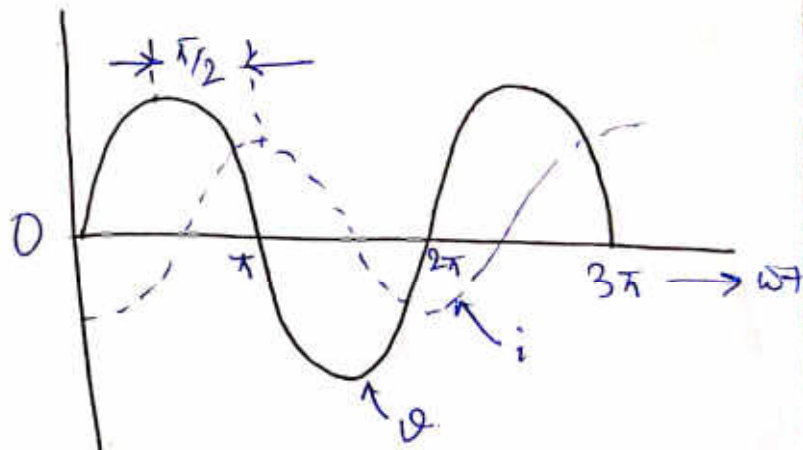

$\cos \phi = 0$ and no power is dissipated in L.


(iii) Pure Capacitance

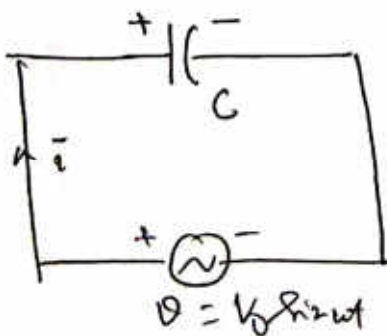

$\omega C \sim R$

Capacitive reactance.

SC-path

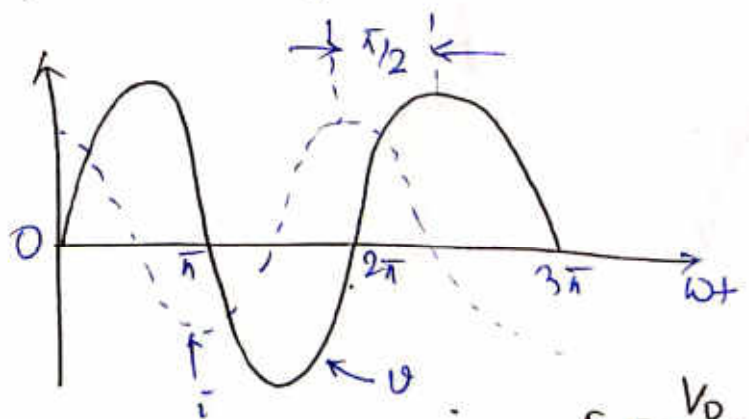

$$q = Cv = CV_0 \sin \omega t$$

$$i = \frac{dq}{dt} = \omega CV_0 \cos \omega t = I_0 \sin(\omega t + \pi/2)$$

$$I_0 = \frac{V_0}{1/\omega C}$$


Blocking Capacitor

Lecture Series (7)

Representation of Sinusoids by Complex Numbers

$$e^{j\omega t} = \cos \omega t + j \sin \omega t \quad (j = \sqrt{-1})$$
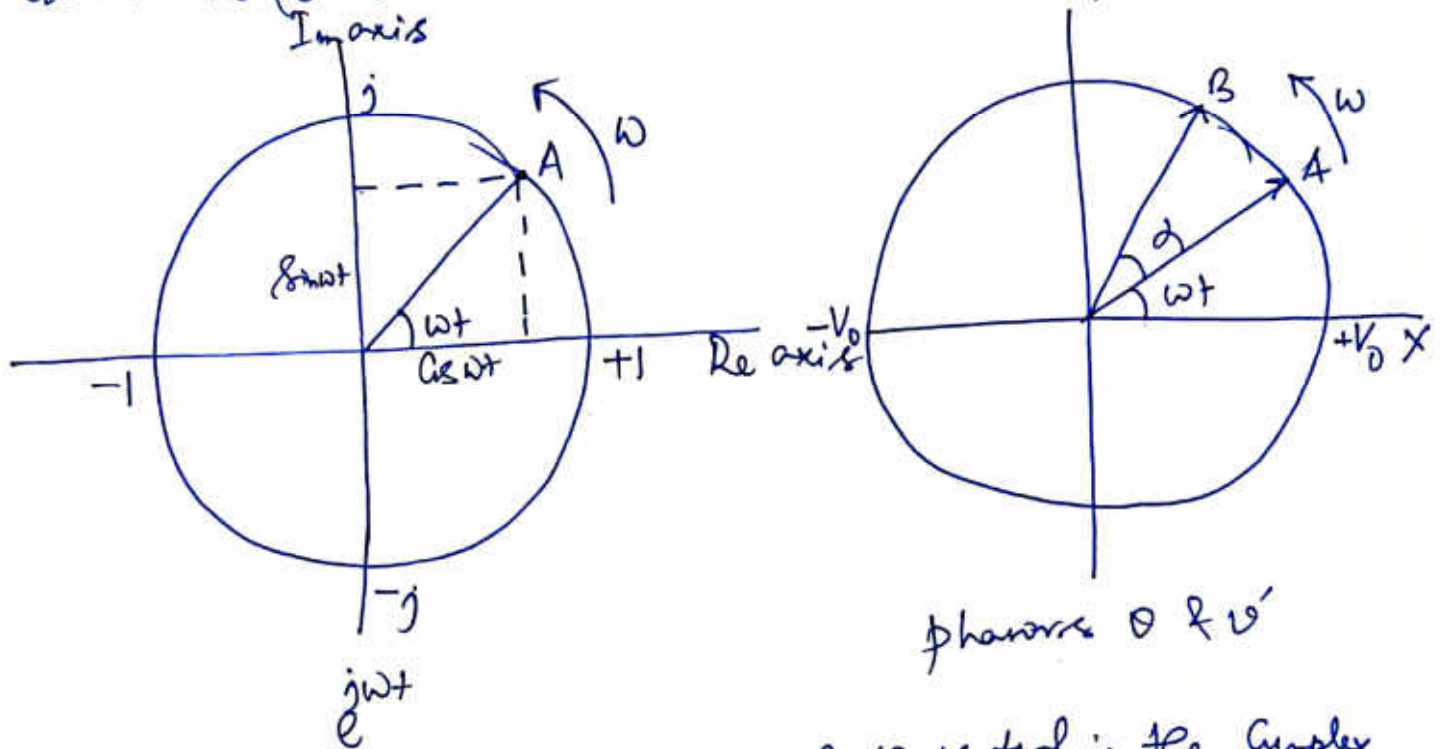
$$\cos \omega t = \operatorname{Re}(e^{j\omega t}) \quad \& \quad \sin \omega t = \operatorname{Im}(e^{j\omega t})$$



Harmonical Vol & Currents can be represented in the Complex plane by radius vectors having a magnitude and a phase w.r.t. a ref angle. Such radius vectors, representing complex no. are known as phasors.

$$v(t) = V_0 \sin \omega t = \operatorname{Im}(V_0 e^{j\omega t}) \quad \vec{OA}$$

$$v'(t) = V_0 \sin(\omega t + \alpha) = \operatorname{Im}(V_0 e^{j(\omega t + \alpha)}) \quad \vec{OB}$$

polar repⁿ:


$$z_1 = |z_1| e^{j\theta} = a e^{j\theta} = a \angle \theta \quad \text{modulus or magnitude } a, \theta \text{ argument, } \angle AOX = \theta$$

$z_2 = z_1 e^{j\phi}$ has the same magnitude a & it leads z_1 by the angle ϕ . If $\phi = \pi/2$

$$\text{then } z_2 = j z_1, \text{ since } e^{j\pi/2} = \cos \pi/2 + j \sin \pi/2 = j$$

multiplication by j means adv of phase by $\pi/2$ or 90° .

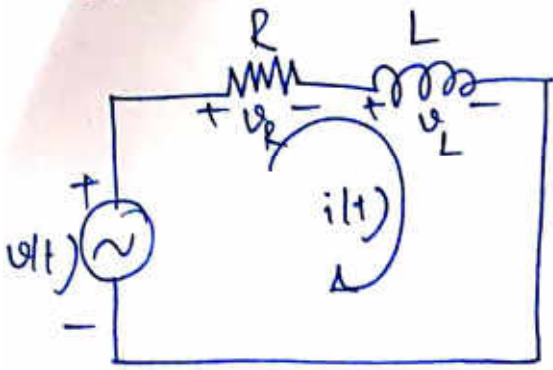Sinusoidal Voltage Applied to a Series RL Circuit



$$Ri + L \frac{di}{dt} = v(t), \quad v(t) = V_0 \cos \omega t$$

$$Ri_r + L \frac{di_r}{dt} = V_0 \cos \omega t \quad \text{Sol}^n \text{ of current } i_r$$

$$Ri_i + L \frac{di_i}{dt} = V_0 \sin \omega t \quad \text{Sol}^n \text{ for the current } i_i$$

Addition (+)

$$i = i_r + j i_i$$

$$Ri + L \frac{di}{dt} = V_0 e^{j\omega t}$$

$$(R + j\omega L)A = V_0 \Rightarrow A = \frac{V_0}{R + j\omega L} = \frac{V_0}{|Z|}$$

$Z (= R + j\omega L)$ impedance of the circuit, $|Z| = \sqrt{R^2 + \omega^2 L^2}$, $\tan \theta = \frac{\omega L}{R}$

$$Z = R + j\omega L = |Z| e^{j\theta}$$

$$i = i_r + j i_i = A e^{j\omega t} = \frac{V_0}{Z} e^{j\omega t} = \frac{V_0}{|Z|} e^{j(\omega t - \theta)}$$

If $v(t) = V_0 \cos \omega t = \text{Re}(V_0 e^{j\omega t})$ if $v(t) = V_0 \sin \omega t = \text{Im}(V_0 e^{j\omega t})$


$$i_r = \frac{V_0}{|Z|} \cos(\omega t - \theta) \quad i_i = \frac{V_0}{|Z|} \sin(\omega t - \theta)$$

Current in a series RL circuit lags the applied voltage by θ .

Reciprocal of Z is called admittance Y .

$$Y = \frac{1}{Z} = \frac{1}{R + j\omega L}$$


Putting $I_0 = \frac{V_0}{|Z|}$ * $\frac{V_0}{|Z|} e^{-j\theta} = I_0 e^{-j\theta}$

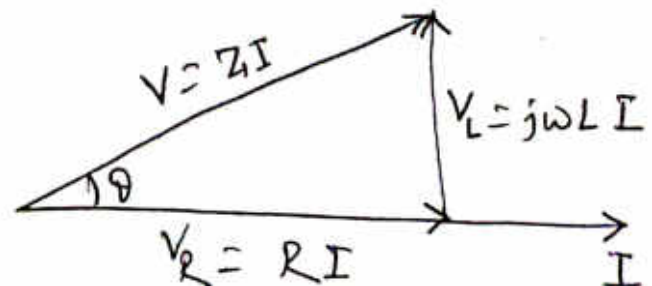

$$|V| = V_0/\sqrt{2} \quad \text{and} \quad |I| = I_0/\sqrt{2}$$

$$\frac{|V| e^{j\theta}}{|Z| e^{j\phi}} = |I| e^{-j\theta} \quad \text{or} \quad \frac{V}{Z} = I$$

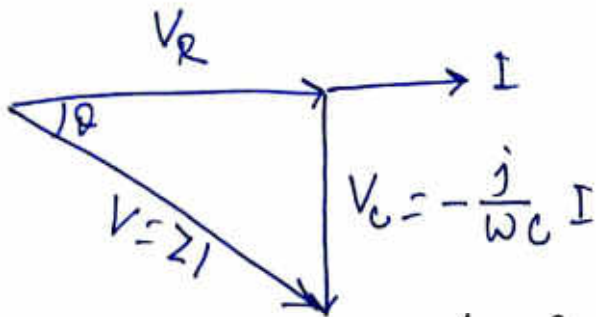Homework: Sinusoidal Vol app to a Series RLC Circuit
 phasor eqⁿ rep^m a gen. Ohm's law




$$Z = [R - \frac{j}{\omega C}]$$

Sinusoidal Voltage Applied to a Series RLC Circuit

$$Ri + L \frac{di}{dt} + \frac{q}{C} = V_0 e^{j\omega t}$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = j\omega V_0 e^{j\omega t}$$

$$i = A e^{j\omega t}$$

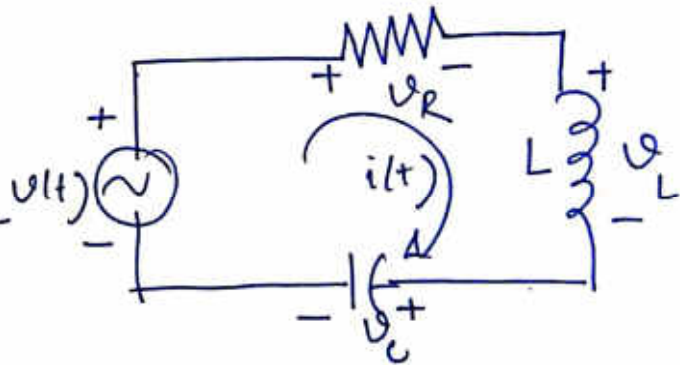

$$\left(-\omega^2 L + j\omega R + \frac{1}{C}\right) A = j\omega V_0$$

$$\left(R + j\omega L + \frac{1}{j\omega C}\right) A = V_0$$

Steady State Current, $i = \frac{V_0 e^{j\omega t}}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$

The impedance $Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = |Z| e^{j\theta}$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\tan \theta = \frac{\left(\omega L - \frac{1}{\omega C}\right)}{R} = \frac{X}{R} \quad X = \left[\omega L - \frac{1}{\omega C}\right]$$



$$i = \frac{V_0}{|Z|} e^{j(\omega t - \theta)}$$

Putting $|I| = \frac{V_0}{|Z|}$ and using r.m.s. values $|I| = \frac{I_0}{\sqrt{2}}$ & $|V| = \frac{V_0}{\sqrt{2}}$


$$|I| e^{-j\theta} = \frac{|V| e^{j0}}{|Z| e^{j\theta}} \quad \text{or } V = ZI$$

Case I: $\omega L > \frac{1}{\omega C}$

Case II: $\omega L < \frac{1}{\omega C}$

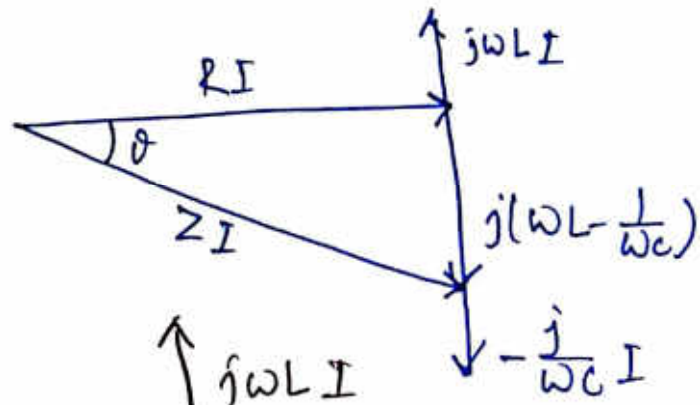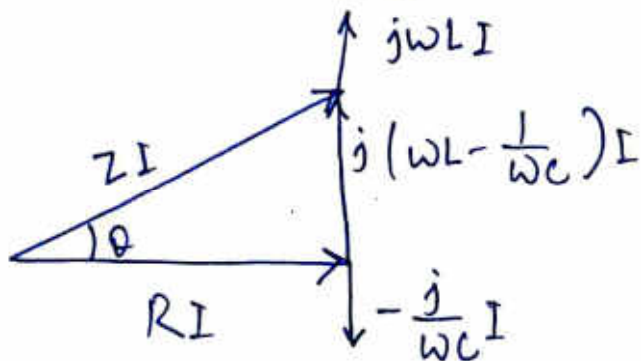

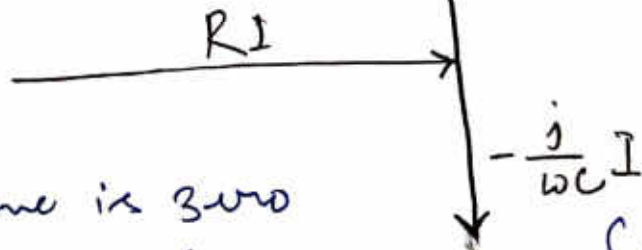
Case III: $\omega L = \frac{1}{\omega C}$




reactance is zero

Circuit is purely resistive.

Series Resonance

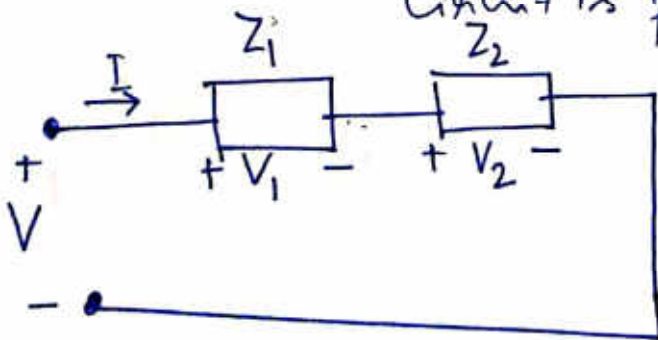
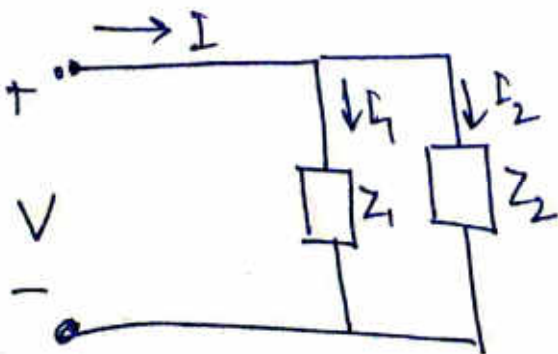
$$Z = Z_1 + Z_2 + Z_3 + \dots + Z_n = \sum_{i=1}^n Z_i$$



$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} = \sum_{i=1}^n \frac{1}{Z_i}$$

$$Y = Y_1 + Y_2 + \dots + Y_n = \sum_{i=1}^n Y_i$$

Series Resonance

The impedance of a series RLC circuit

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

The condition for resonance, setting reactance term to zero



$$\omega L - \frac{1}{\omega C} = 0 \quad \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

The impedance at resonance is R , while at off-resonant frequency the impedance has the magnitude

$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

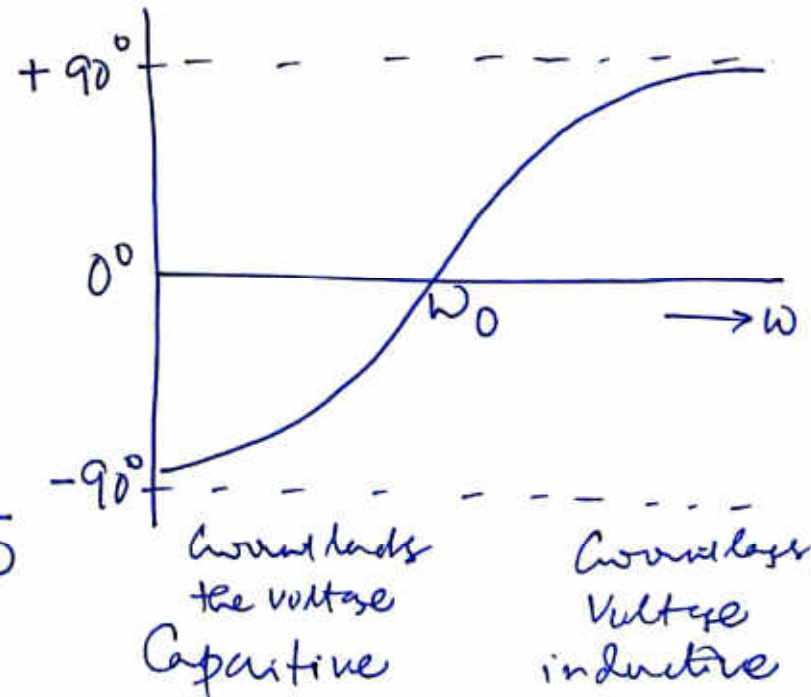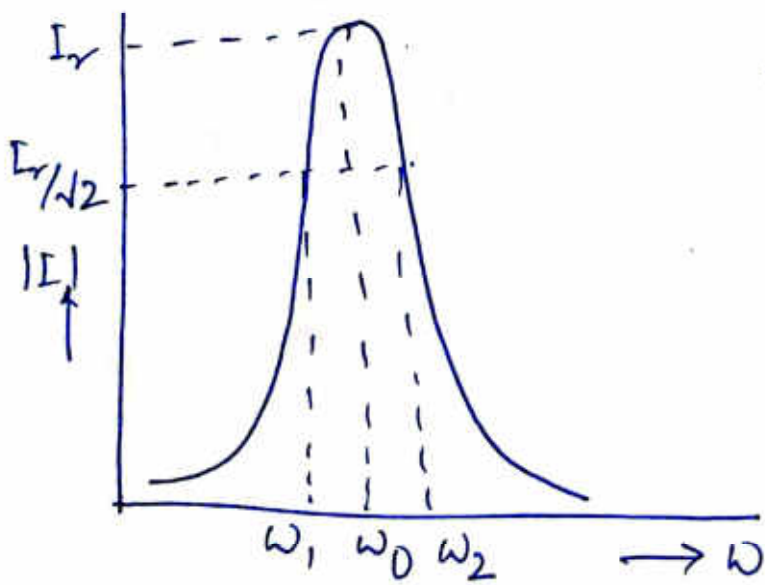As the current response of the series circuit is maximum at resonance, the circuit is sometimes called an acceptor circuit.



$$\omega \approx \omega_0, \quad \theta = 0, \quad \text{resistive}$$